



# INDIAN SCHOOL MUSCAT

## SECOND PERIODIC ASSESSMENT

### PHYSICS

CLASS: 12

Sub.Code: 042

Time Allotted: 50mts.

19.05.2019

Max .Marks: 20

#### GENERAL INSTRUCTIONS:

All questions are compulsory.


There are 11 questions in all.


Question no 1 to 5 carry one mark each.

Question no 6 to 18 carry two marks each.

Question no 9 to 11 carry three marks each.

$$\frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ Nm}^2 \text{ C}^{-2} \text{ N} \quad \epsilon_0 = 8.854 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$$

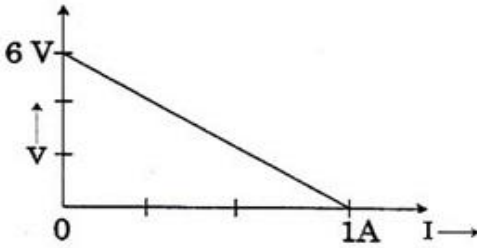1.	How does the energy stored in a capacitor change if the plates of a charged capacitor are moved farther, the battery remaining connected?	1
2.	Define electrical conductance of a conductor and give its SI unit.	1
3.	Two materials Si and Cu, are cooled from 300 K to 60 K. What will be the effect on their resistivity?	1
4.	Express dielectric constant of a medium in terms of capacitance. What is its SI unit?	1
5.	What do you mean by dielectric strength of a dielectric?	1
6.	Derive an expression for the energy stored in a parallel plate capacitor C, charged to a potential difference V.	2
7.	<p>The plot of the variation of potential difference across a combination of three identical cells in series, versus current is shown in figure. What is the emf and internal resistance of each cell?</p> 	2

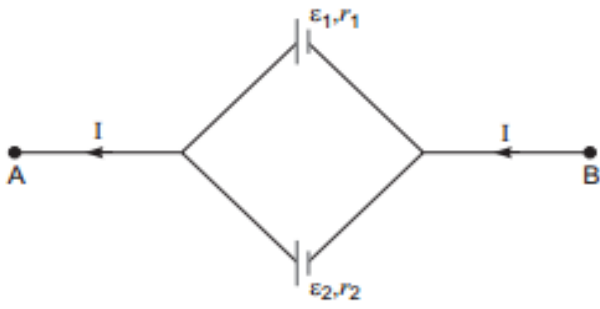8.	Two conducting wires <b>X</b> and <b>Y</b> of same diameter but different materials are joined in series across a battery. If the number density of electrons in <b>X</b> is twice that in <b>Y</b> , find the ratio of drift velocity of electrons in the two wires.	2
9.	Derive an expression for drift velocity of free electrons in a conductor in terms of relaxation time of electron.	3
10.	Two cells of emfs $E_1$ and $E_2$ having internal resistances $r_1$ and $r_2$ respectively are connected in parallel as shown. Deduce the expressions for the equivalent emf and equivalent internal resistance of a cell which can replace the combination between the points <b>A</b> and <b>B</b> .	3
		
11.	Two parallel plate capacitors <b>X</b> and <b>Y</b> have the same area of plates and same separation between them. <b>X</b> has air between the plates while <b>Y</b> contains a dielectric medium of $\epsilon_r = 4$ (i) Calculate the capacitance of each capacitor if equivalent capacitance of the combination is <b>4</b> microfarad. (ii) Calculate the potential difference between plate X and Y.	3
