



**INDIAN SCHOOL MUSCAT
MIDDLE SECTION**



SUBJECT: SCIENCE

REVISION WORKSHEET#8

TOPIC: ELECTRICITY AND CIRCUITS.

STD VI

RESOURCE PERSON: Mr. SASIKUMAR K P

DATE: /10/18

Name of the student _____ Sec _____ Roll no _____

Answer the following questions.

Q.1. Which are the two terminals of a cell?

Q.2. How does a cell produce electricity?

Q.3. What is the function of filament in an electric bulb?


Q.4. What is the direction of current in an electric circuit?

Q.5. What do you understand when we say that a bulb is fused?

Q.6. Differentiate between a conductor and an insulator.

Q.7. What is the precaution that you must take when you join cells to make a battery?

Q.8. Name the parts labelled A, B and C.

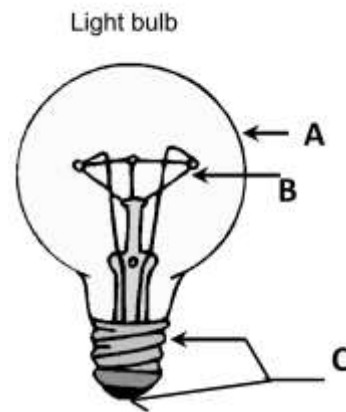

Q.9. Name the parts labelled A, B, C, D, E and F in the following diagram of an electric torch.

